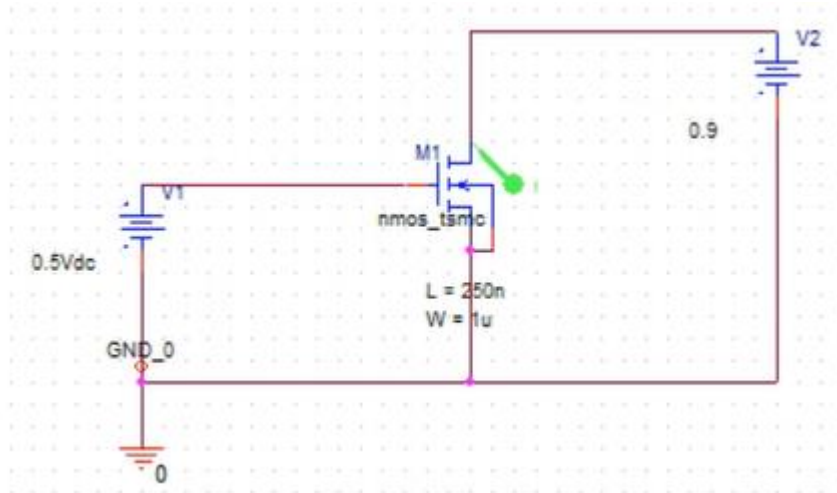


# Prelab 1, Analog Integrated Circuits


Ole Janse, Finn Rautenberg, 29.11.2022, Lübeck

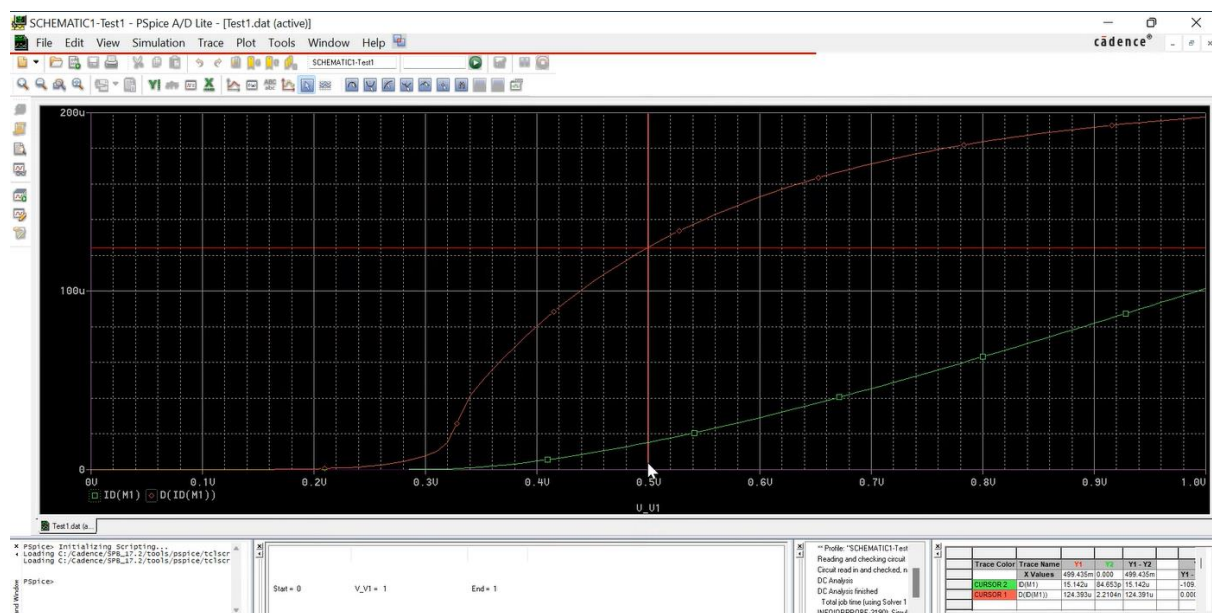f) Task: Determine the transconductance  $g_m$  of the transistor at  $V_{GS} = 0.5 \text{ V}$





Simulation of DC-Sweep of  $G_{gs,dc}$  from 0V to 1V

Plot of  $I_{d,dc}$  and the slope  $g_m = I_{d,dc}/V_{gs,dc}$  at  $G_{gs,dc}=0.5\text{V}$  by  $D(I(IM1))$



$g_m = 124 \mu\text{S}$  @  $V_{gs,dc}=0.5\text{V}$

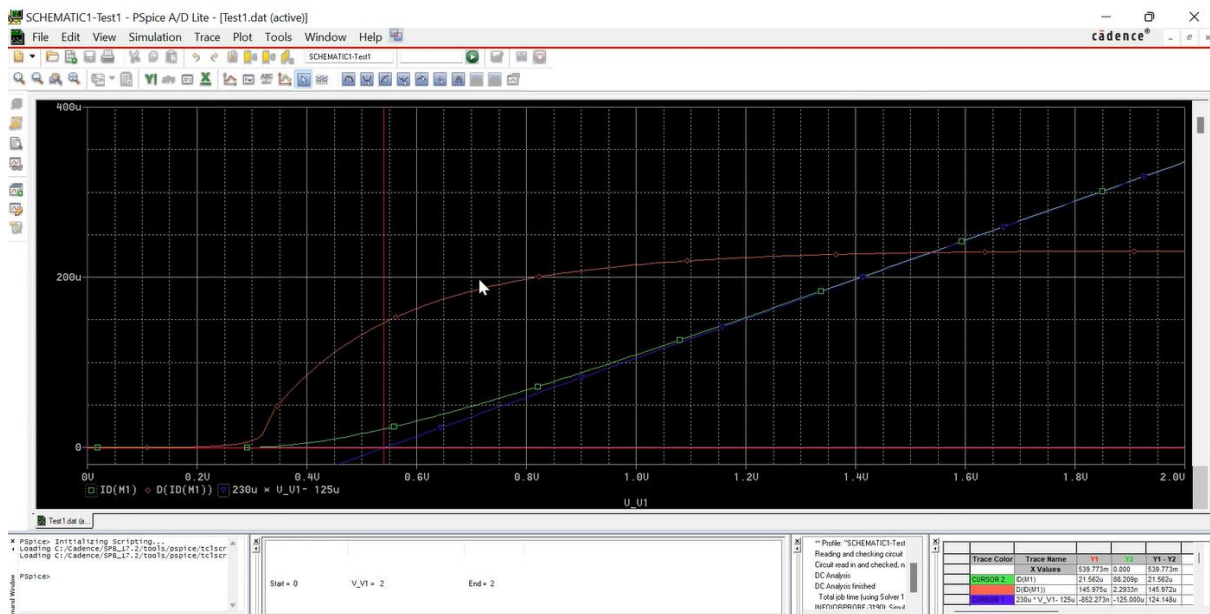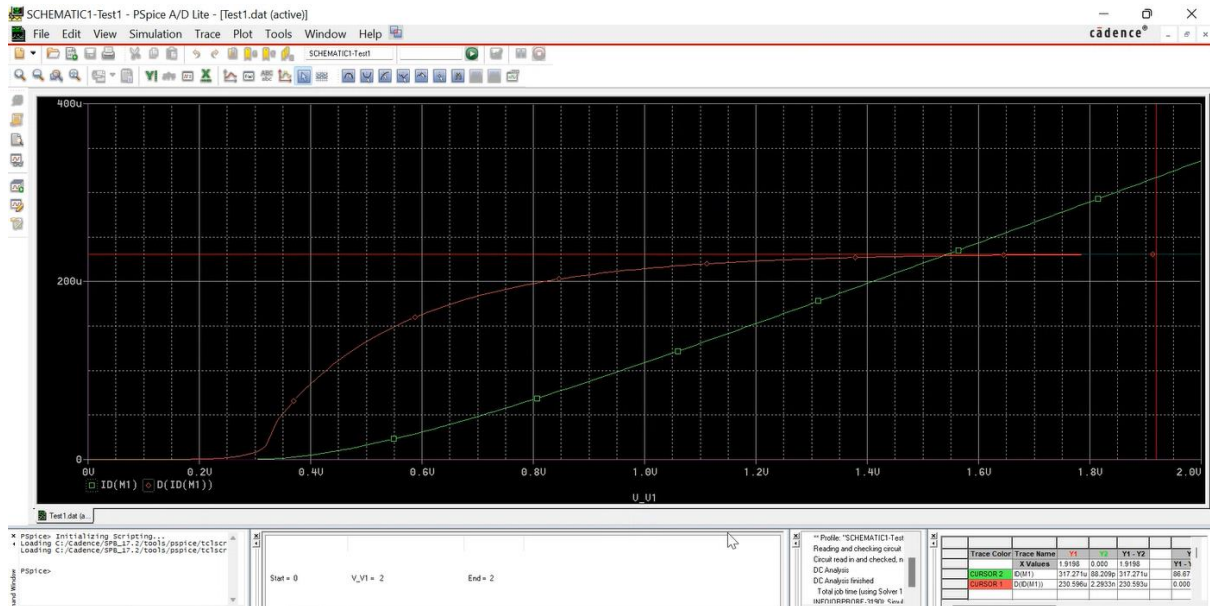g) Task: Determine the transistor  $V_{th}$  value by sketching the tangent line at the highest slope of  $I_{d,dc}/V_{gs,dc}$  and determine the voltage of  $U_{gs,dc}$  at  $I_{d,dc}=0A$  of the tangent



i) Task: Determine the linear (triode) region of the transistor

To satisfy linear region

- $V_{gs,dc} < V_{th} = 539\text{mV} \rightarrow$  always fulfilled because  $V_{gs,dc} = 500\text{mV} < 539\text{mV}$
- and  $V_{ds,dc} < V_{gs,dc} - V_{th} = 500\text{mV} - 539\text{mV} = -39\text{mV}$  (Sim zeigt das bis  $\sim 164\text{mV}$  ende von  $V_{ds,dc}$  linearer Bereich :/ Ist  $V_{th}$  oder Formel falsch?)

Simulation of DC-Sweep of  $G_{ds,dc}$  from 0V to 2V

Plot of  $I_{d,dc}$

$V_{pinch,off} \sim 150\text{mV}$




j) Task: Determin small signal output resistance  $r_{ds} = r_o$ . Determine slope  $r_o = I_{d,dc}/D_{ds,dc}$


- $r_{ds} = 5,10 \text{ k}\Omega$  @  $V_{ds,dc} = 0\text{V}$
- $r_{ds} = 8,41 \text{ k}\Omega$  @  $V_{ds,dc} = 50\text{mV}$
- $r_{ds} = 515,4 \text{ k}\Omega$  @  $V_{ds,dc} = 0,9\text{V}$

Simulation of DC-Sweep of  $G_{ds,dc}$  from 0V to 2V

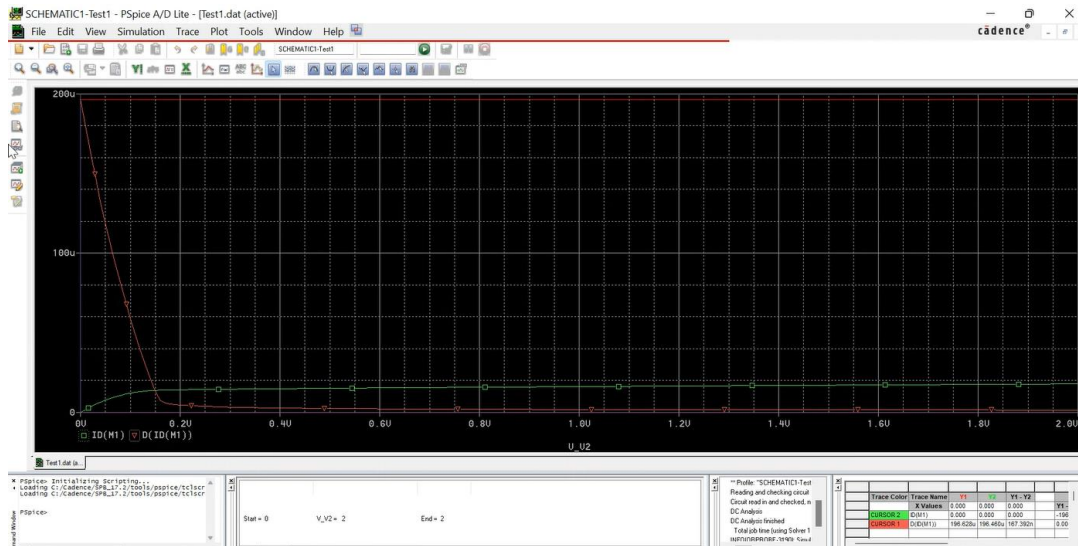Plot of  $I_{d,dc}$  and Derivation  $D(I_D(M1))$



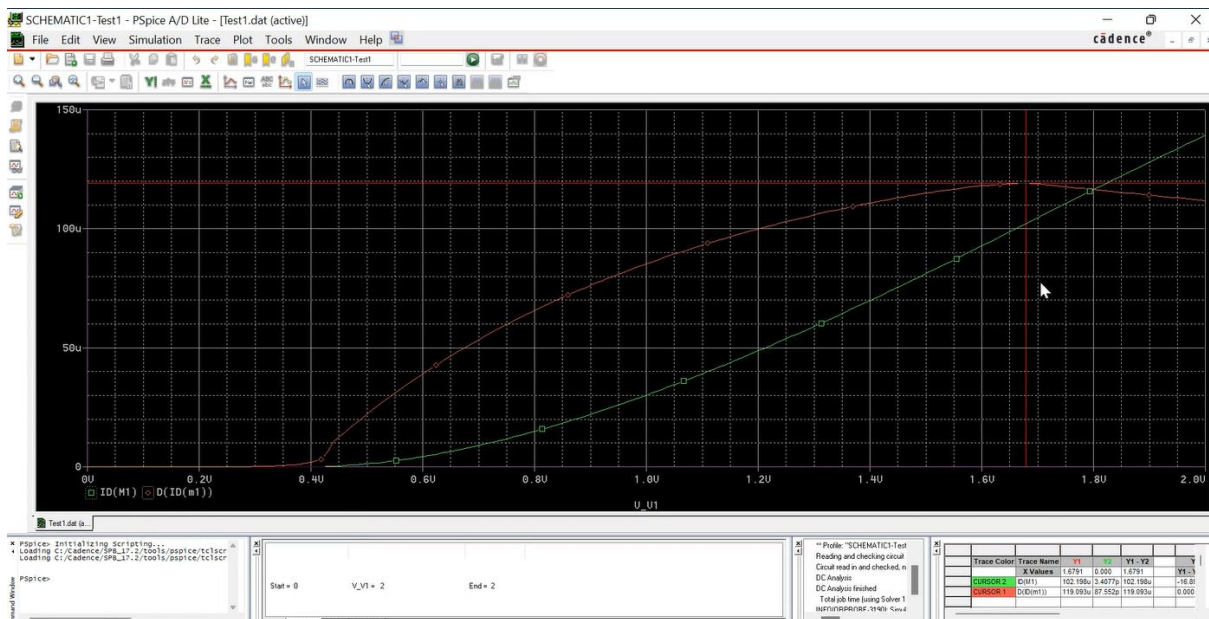k) Task: Repeat for  $L=1\mu\text{m}$  j)




The highest slope was determined at  $V_{gs,dc}=1,67\text{V}$  with  $g_m=119\text{ uS}$

New threshold value  $813\text{mV}$


To satisfy linear region

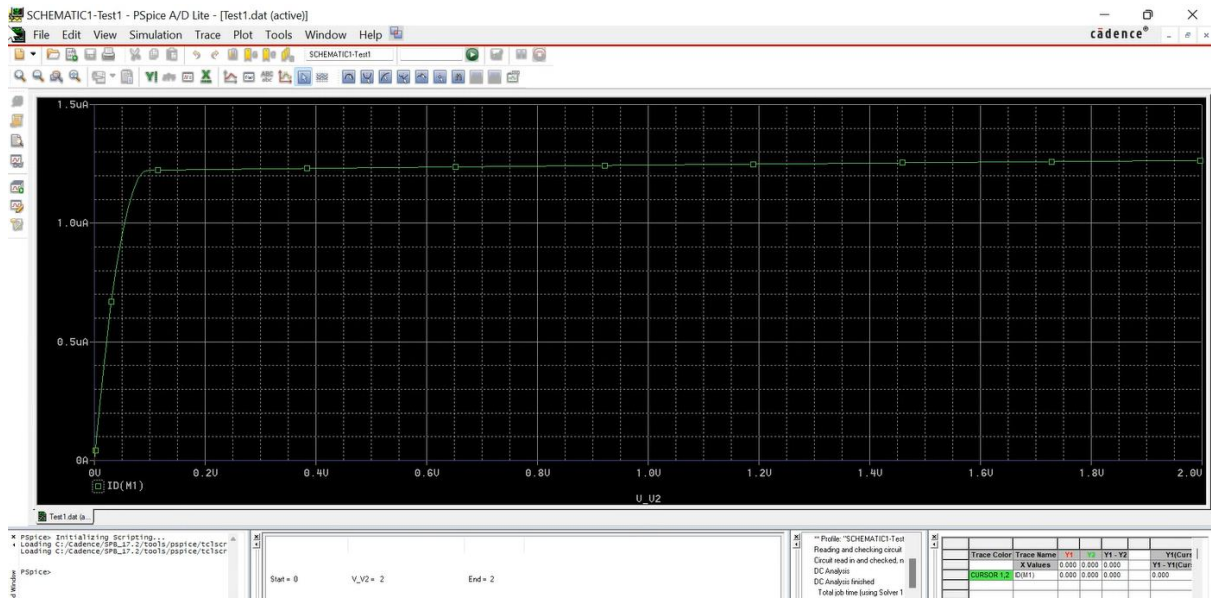- $V_{gs,dc} < V_{th} = 813\text{mV} \rightarrow$  always fulfilled because  $V_{gs,dc} = 500\text{mV} < 813\text{mV}$
- and  $V_{ds,dc} < V_{gs,dc} - V_{th} = 500\text{mV} - 813\text{mV} = -313\text{mV}$





$V_{pinch,off} \sim 100mV$

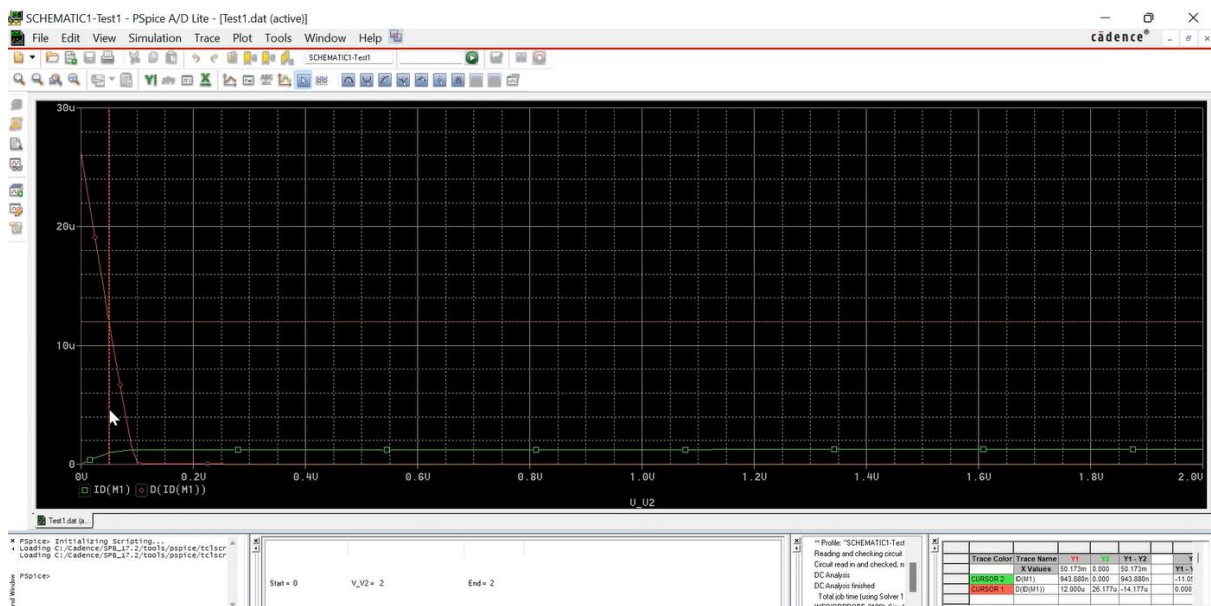

$r_0 = 45,8 \text{ MOhm}$ , lower channel length modulation as expected

l) Task: Determin  $I_{d,dc}$  for steady state by simulation, switched back to  $L=250\text{nm}$

What todo??

m) Task: Compare values of dc sweep and bias point simulation

	Sim DC-sweep	Sim Bias Point ( $V_{gs,dc}=0,9\text{V}$ )
$V_{th}$	539mV	328mV
$G_m$	230 $\mu\text{S}$	132 $\mu\text{S}$
$r_o$	515 kOhm	512 kOhm

Deviation on  $V_{th}$  and  $g_m$  due to selection on  $V_{ds,dc} \neq 0,9\text{V}$  as in bias point simulation